 


Estimating Delays

- ▶ Would be nice to have a “back of the envelope” method for sizing gates for speed
- ▶ Logical Effort
 - ▶ Book by Sutherland, Sproull, Harris
 - ▶ Chapter 1 is on our web page



Gate Delay Model

- ▶ First, normalize a model of delay to dimensionless units to isolate fabrication effects
 - ▶ $d_{abs} = d \tau$
 - ▶ τ is the delay of a minimum inverter driving another minimum inverter with no parasitics
 - ▶ In a 0.6u process, this is approx 40ps
 - ▶ Now we can think about delay in terms of d and scale it to whatever process we're building the circuit in

Gate Delay


- ▶ Delay of a gate d has two components
 - ▶ A fixed part called *parasitic delay* p
 - ▶ A part proportional to the load on the output called the *effort delay* or *stage effort* f
 - ▶ **Total delay** is measured in units of τ , and is sum of these delays
 - ▶ $d = f + p$

Effort Delay

- ▶ The **effort delay** (due to load) can be further broken down into two terms
 - ▶ $f = g * h$
 - ▶ $g =$ **logical effort** which captures properties of the gate's structure
 - ▶ $h =$ **electrical effort** which captures properties of load and transistor sizes
 - ▶ $h = C_{out}/C_{in}$
 - ▶ C_{out} is capacitance that loads the output
 - ▶ C_{in} is capacitance presented at the input
 - ▶ So, $d = gh + p$


Logical Effort

 - ▶ Logical effort normalizes the output drive capability of a gate to match a unit inverter
- ▶ How much more input capacitance does a gate need to present to offer the same drive as in inverter?



Computing Logical Effort

 - ▶ DEF: *Logical effort is the ratio of the input capacitance of a gate to the input capacitance of an inverter delivering the same output current.*
- ▶ Measure from delay vs. fanout plots
- ▶ Or estimate by counting transistor widths



Logical Effort of Other Gates

- ▶ Logical effort of common gates assuming that P/N size ratio is 2

Gate Type	Number of inputs					
	1	2	3	4	5	n
<i>Inverter</i>	1					
<i>NAND</i>		4/3	5/3	6/3	7/3	$(n+2)/3$
<i>NOR</i>		5/3	7/3	9/3	11/3	$(2n+1)/3$
<i>MUX</i>		2	2	2	2	2
<i>XOR</i>		4	12	32		


Electrical Effort

- ▶ Value of **logical effort** g is independent of transistor size
 - ▶ It's related to the ratios and the topology
- ▶ **Electrical effort** h captures the drive capability of the transistors via sizing
 - ▶ Electrical effort $h = C_{out}/C_{in}$
 - ▶ Note that as transistor sizes for a gate increase, h decreases because C_{in} goes up

Parasitic Delay


- ▶ Parasitic delay p is caused by the internal capacitance of the gate
 - ▶ It's constant and independent of transistor size
 - ▶ As you increase the transistor size, you also increase the cap of the gate/source/drain areas which keeps it constant
 - ▶ For our purposes, normalize p_{inv} to 1
 - ▶ N-input NAND = $n \cdot p_{inv}$
 - ▶ N-input NOR = $n \cdot p_{inv}$
 - ▶ N-way mux = $2n \cdot p_{inv}$
 - ▶ XOR = $4 \cdot p_{inv}$

Plots of Gate Delay

 

Delay Estimation

Delay Estimation

 


Remember, τ in
Our process $\sim 40\text{ps}$

$$A_delay = g \cdot h + p = 1 \cdot (\text{CinB}/\text{CinA}) + 1$$

$$= 1 \cdot (4 \cdot \text{CinA}/\text{CinA}) + 1 = 4 + 1 = 5 \text{ time units}$$

$\sim 200\text{ps}$

 

$$A_delay = g \cdot h + p = (4/3) \cdot (\text{CinB}/\text{CinA}) + 2 \cdot 1$$

$$\text{Cin}_B = 4 \cdot 3 = 12. \quad \text{Cin}_A = 4$$


$$A_delay = (4/3) \cdot (12/4) + 2 = 4 + 2 = 6 \text{ units} \quad \sim 240\text{ps}$$

Nand2 worse because of higher parasitic delay than inverter.

Note that $g \cdot h$ term was same for both because NAND2 sized to provide same current drive.

Delay Estimation


Delay Estimation

 

Remember, τ in
Our process $\sim 40\text{ps}$

$$A_delay = g \cdot h + p = 1 \cdot (\text{CinB}/\text{CinA}) + 1 \quad \sim 200\text{ps}$$
 
$$= 1 \cdot (4 \cdot \text{CinA}/\text{CinA}) + 1 = 4 + 1 = 5 \text{ time units}$$



τ in 180nm = $\sim 12\text{ps}$
FO4 Inverter delay = 60ps
FO4 NAND delay = 72ps

$$A_delay = g \cdot h + p = (4/3) \cdot (\text{CinB}/\text{CinA}) + 2 \cdot 1$$

$$\text{Cin}_B = 4 \cdot 3 = 12. \quad \text{Cin}_A = 4$$


$$A_delay = (4/3) \cdot (12/4) + 2 = 4 + 2 = 6 \text{ units} \quad \sim 240\text{ps}$$

Nand2 worse because of higher parasitic delay than inverter.

Note that $g \cdot h$ term was same for both because NAND2 sized to provide same current drive.

 Example: Ring Oscillator


- ▶ Estimate the frequency of an N-stage ring oscillator



Logical Effort: $g =$
Electrical Effort: $h =$
Parasitic Delay: $p =$
Stage Delay: $d =$
Period of osc =

 Example: Ring Oscillator


- ▶ Estimate the frequency of an N-stage ring oscillator



Logical Effort: $g = 1$
Electrical Effort: $h = 1$
Parasitic Delay: $p = 1$
Stage Delay: $d = 2$ so $d_{\text{abs}} = 80\text{ps}$
Period: $2 \cdot N \cdot d_{\text{abs}} = 4.96\text{ns}$, Freq = $\sim 200\text{MHz}$

 Example: FO4 Inverter


- ▶ Estimate the delay of a fanout-of-4 (FO4) inverter



Logical Effort: $g =$
 Electrical Effort: $h =$
 Parasitic Delay: $p =$
 Stage Delay: $d =$

 Example: FO4 Inverter


- ▶ Estimate the delay of a fanout-of-4 (FO4) inverter



Logical Effort: $g = 1$
 Electrical Effort: $h = 4$
 Parasitic Delay: $p = 1$
 Stage Delay: $d = gh + p = 5$

The FO4 delay is about
 200 ps in 0.6 μm process
 60 ps in a 180 nm process
 $f/3$ ns in an $f \mu\text{m}$ process

Delay Estimation

 


- ▶ If $C_{in} = x$, $C_{out} = 10x$, thus $h = 10$
- ▶ $g = 9/3 = 3$
- ▶ $d = gh + p = 3 \cdot 10 + 4 \cdot 1 = 34$ (1360 ps)

Multi Stage Delay

MultiStage Delay

 - Recall rule of thumb that said to balance the delay at each stage along a critical path
- Concepts of logical effort and electrical effort can be generalized to multistage paths



$$\text{Path logical effort} = g_1 * g_2 * g_3 * g_4$$


$$\text{In general, Path logic effort } G = \prod g(i)$$

$$\text{Path electrical effort } H = C_{out} / C_{in_{\text{first_gate}}}$$

Must remember that electrical effort only is concerned with effect of logic network on input drivers and output load.

Off-Path Load

Off Path Load

 

Off path load will divert electrical effort from the main path, must account for this. Define a *branching effort* b as:

$$b = (\text{Con}_{\text{path}} + \text{Coff}_{\text{path}}) / \text{Con}_{\text{path}} \quad \frac{C_{\text{total}}}{C_{\text{useful}}}$$

The branching effort will modify the electrical effort needed at that stage. The branch effort B of the path is:

$$B = \prod b(i)$$

Summary – multistage networks

▶ Logical effort generalizes to multistage networks

▶ *Path Logical Effort* $G = \prod g_i$

▶ *Path Electrical Effort* $H = \frac{C_{\text{out-path}}}{C_{\text{in-path}}}$

▶ *Path Effort* $F = \prod f_i = \prod g_i h_i$

▶ Can we write $F = GH$?

Branching Effort

- ▶ Remember *branching effort*
 - ▶ Accounts for branching between stages in path

$$b = \frac{C_{\text{on path}} + C_{\text{off path}}}{C_{\text{on path}}}$$

$$B = \prod b_i$$

Note:

$$\prod h_i = BH$$

- ▶ Now we compute the path effort
 - ▶ $F = GBH$

Multistage Delays

- ▶ Path Effort Delay $D_F = \sum f_i$

- ▶ Path Parasitic Delay $P = \sum p_i$

- ▶ Path Delay $D = \sum d_i = D_F + P$

Designing Fast Circuits

$$D = \sum d_i = D_F + P$$

Delay is smallest when each stage bears same effort

$$\hat{f} = g_i h_i = F^{\frac{1}{N}}$$

Thus minimum delay of N stage path is

$$D = NF^{\frac{1}{N}} + P$$

This is a **key** result of logical effort

- ▶ Find fastest possible delay
- ▶ Doesn't require calculating gate sizes

Minimizing Path Delay

The absolute delay will have the parasitic delays of each stage summed together.

However, can *focus on just Path effort F* for minimization purposes since parasitic delays are constant.

For an N-stage network, *the path delay is least when each stage in the path bears the same stage effort.*

$$f(\min) = g(i) * h(i) = F^{1/N}$$

Minimum achievable path delay

$$D(\min) = N * F^{1/N} + P$$

Note that if N=1, then $d = f + p$, the original single gate equation.

Choosing Transistor Sizes

Remember that the stage effort $h(i)$ is related to transistor sizes.

$$f(\min) = g(i) * h(i) = F^{1/N}$$

So


$$h(i) \min = F^{1/N} / g(i)$$

To size transistors, start at end of path, and compute:

$$C_{in}(i) = g_i * C_{out}(i) / f(\min)$$

Once $C_{in}(i)$ is know, can distribute this among transistors of that stage.

Example

 

Size the transistors of the nand2 gates for the three stages shown.

$$\text{Path logic effort} = G = g_0 * g_1 * g_2 = 4/3 * 4/3 * 4/3 = 2.37$$

$$\text{Branching effort } B = 1.0 \text{ (no off-path load)}$$

$$\text{Electrical effort } H = C_{out}/C_{in} = C/C = 1.0$$

$$\begin{aligned} \text{Min delay achievable} &= 3 * (G*B*H)^{1/3} + 3 * (2 * p_{inv}) \\ &= 3 * (2.37 * 1 * 1)^{1/3} + 3 * (2 * 1.0) = 10.0 \end{aligned}$$

$$\min D = N * F^{1/N} + P$$

Example, continued

The effort of each stage will be:

$$f_{\min} = (G \cdot B \cdot H)^{1/3} = (2.37 \cdot 1.0 \cdot 1.0)^{1/3} = 1.33 = 4/3$$

Cin of last gate should equal:


$$\begin{aligned} C_{\text{in last gate (min)}} &= g_i \cdot C_{\text{out (i)}} / f_{\min} \\ &= 4/3 \cdot C / (4/3) = C \end{aligned}$$

Cin of middle gate should equal:

$$\begin{aligned} C_{\text{in middle gate}} &= g_i \cdot C_{\text{in last gate}} / f_{\min} \\ &= 4/3 \cdot C / (4/3) = C \end{aligned}$$

All gates have same input capacitance, distribute it among transistors.

Transistor Sizes for Example

 


Where gate capacitance of
 $2 \cdot W \cdot L$ Mosfet = $C/2$

Choose W accordingly.

Another Example, Larger Load

Let Load = $8C$, what changes?

 

Size the transistors of the nand2 gates for the three stages shown.

$$\text{Path logic effort} = G = g_0 * g_1 * g_2 = 4/3 * 4/3 * 4/3 = 2.37$$

Branching effort $B = 1.0$ (no off-path load)

$$\text{Electrical effort } H = C_{out}/C_{in} = 8C/C = 8.0$$

$$\begin{aligned} \text{Min delay achievable} &= 3 * (G*B*H)^{1/3} + 3 (2 * \text{pinv}) \\ &= 3 * (2.37 * 1 * 8)^{1/3} + 3 (2 * 1.0) = 14.0 \end{aligned}$$

8C Load Example Cont.

The effort of each stage will be:

$$f_{\min} = (G*B*H)^{1/3} = (2.37 * 1.0 * 8)^{1/3} = 2.67 = 8/3$$

C_{in} of last gate should equal:

$$\begin{aligned} C_{in \text{ last gate (min)}} &= g_i * C_{out (i)} / f(\min) \\ &= 4/3 * 8C / (8/3) = 4C \end{aligned}$$


C_{in} of middle gate should equal:

$$\begin{aligned} C_{in \text{ middle gate}} &= g_i * C_{in \text{ last gate}} / f(\min) \\ &= 4/3 * 4C / (8/3) = 2C \end{aligned}$$

Note that each stage gets progressively larger, as is typical with a multi-stage path driving a large load.

Example 1.6 from Chap 1

Size path from
A to B

 

Path logic effort $G = g_0 * g_1 * g_2 = 4/3 * 4/3 * 4/3 = 2.37$

Branch effort, 1st stage $= (y+y)/y = 2$.

Branch effort, 2nd stage $= (z+z+z)/z = 3$

Path Branch effort $B = 2 * 3 = 6$.

Path electrical effort $H = C_{out}/C_{in} = 4.5C/C = 4.5$

Path stage effort $= F = G*B*H = 2.37*6*4.5 = 64$.

Min delay $= N(F)^{1/N} + P = 3*(64)^{1/3} + 3(2\text{pinv}) = 18.0$ units

Example 1.6 Continued

Stage effort of each stage should be:

$$f(\text{min}) = (F)^{1/N} = (GBH)^{1/N} = (64)^{1/3} = 4$$

Determine C_{in} of last stage:

$$C_{in}(z) = g * C_{out} / f(\text{min}) = 4/3 * 4.5C / 4 = 1.5 C$$

Determine C_{in} of middle stage:

$$C_{in}(y) = g * (3*C_{in}(z)) / f(\text{min}) = 4/3 * (3*1.5C) / 4 = 1.5C$$


Is first stage correct?

$$C_{in}(A) = g * (2*C_{in}(y)) / f(\text{min}) = 4/3 * (2*1.5C) / 4 = C$$


Yes, self-consistent.

 Example: 3-stage path

- ▶ Select gate sizes x and y for least delay from A to B




Example: 3-stage path

 

Logical Effort $G =$
 Electrical Effort $H =$
 Branching Effort $B =$
 Path Effort $F =$
 Best Stage Effort $\hat{f} =$
 Parasitic Delay $P =$
 Delay $D =$

Example: 3-stage path

 

Logical Effort $G = (4/3) * (5/3) * (5/3) = 100/27$

Electrical Effort $H = 45/8$

Branching Effort $B = 3 * 2 = 6$

Path Effort $F = GBH = 125$

Best Stage Effort $\hat{f} = \sqrt[3]{F} = 5$

Parasitic Delay $P = 2 + 3 + 2 = 7$


Delay $D = 3 * 5 + 7 = 22 = 4.4 \text{ FO4}$

Example: 3-stage path

► Work backward for sizes

y =

x =

 


Example: 3-stage path

► Work backward for sizes


$$y = 45 * (5/3) / 5 = 15$$

$$x = (15*2) * (5/3) / 5 = 10$$

 

Example 1.7 from Chap 1

Cin = 10u gate cap

 

Path logic effort $G = g_0 * g_1 * g_2 * g_3 = 1 * 5/3 * 4/3 * 1 = 20/9$

Path Branch effort $B = 1$

Path electrical effort $H = C_{out}/C_{in} = 20/10 = 2$

Path stage effort = $F = G * B * H = (20/9) * 1 * 2 = 40/9$

For Min delay, each stage has effort $(F)^{1/N} = (40/9)^{1/4} = 1.45$

$$z = g * C_{out}/f(\min) = 1 * 20 / 1.45 = 14$$

$$y = g * C_{in}(z) / f(\min) = 4/3 * 14 / 1.45 = 13$$

$$x = g * C_{in}(y) / f(\min) = 5/3 * 13 / 1.45 = 15$$


Note: Don't care about parasitics for gate sizing, only if you want to know absolute delay...

Misc. Comments

- ▶ Note that you never size the first gate
 - ▶ This gate is assumed to be fixed
 - ▶ If you were allowed to size it, the algorithm would try to make it as large as possible
- ▶ This is an estimation algorithm
 - ▶ Authors claim that sizing a gate by 1.5x too big or small still results in a path delay within 15% of minimum




Sensitivity Analysis

 - ▶ How sensitive is delay to using exactly the best number of stages?




- ▶ $2.4 < \rho < 6$ gives delay within 15% of optimal
 - ▶ We can be sloppy!
 - ▶ I like $\rho = 4$

Evaluating Different Options

   

Option #1

 

$$\text{Path logic effort } G = g_0 * g_1 * g_2 = 1 * 6/3 * 1 = 2$$

$$\text{Path Branch effort } B = 1$$

$$\text{Path electrical effort } H = C_{out}/C_{in} = 8C/C = 8$$


$$\text{Path stage effort } = F = G * B * H = 2 * 1 * 8 = 16$$

$$\text{Min delay: } = N * (F)^{1/N} + P$$

$$= 3 * (16)^{1/3} + (p_{inv} + 4 * p_{inv} + p_{inv})$$

$$= 3 * (2.5) + 6 = 13.5$$

Option #2

 

Path logic effort $G = g_0 * g_1 * g_2 = 1 * 4/3 * 5/3 = 20/9$

Path Branch effort $B = 1$

Path electrical effort $H = C_{out}/C_{in} = 8C/C = 8$

Path stage effort $F = G * B * H = 20/9 * 1 * 8 = 160/9$

$$\begin{aligned} \text{Min delay: } &= N * (F)^{1/N} + P \\ &= 3 * (160/9)^{1/3} + (p_{inv} + 2 * p_{inv} + 2 * p_{inv}) \\ &= 3 * 2.6 + 5 = 12.8 \end{aligned}$$

Option #2 appears to be better than Option #1, by a slight margin.

How many stages?

- ▶ Consider three alternatives for driving a load 25 times the input capacitance
 - ▶ One inverter
 - ▶ Three inverters in series
 - ▶ Five inverters in series
- ▶ They all do the job, but which one is fastest?

How many stages?

- ▶ In all cases: $G = 1$, $B = 1$, and $H = 25$
- ▶ Path delay is $N(25)^{1/N} + N P_{inv}$
 - ▶ $N = 1$, $D = 26$ units
 - ▶ $N = 3$, $D = 11.8$ units
 - ▶ $N = 5$, $D = 14.5$ units
- ▶ Since $N=3$ is best, each stage will bear an effort of $(25)^{1/3} = 2.9$
 - ▶ So, each stage is $\sim 3x$ larger than the last
 - ▶ In general, the best stage effort is between 3 and 4 (not e as often stated)
 - ▶ The e value doesn't use parasitics...

Choosing the Best # of Stages

- ▶ You can solve the delay equations to determine the number of stages N that will achieve the minimum delay
 - ▶ Approximate by $\text{Log}_4 F$

<i>Path Effort</i> F	<i>Best</i> N	<i>Min Delay</i> D	<i>Stage effort</i> f
0-5.83	1	1.0-6.8	0-5.8
5.83-22.3	2	6.8-11.4	2.4-4.7
22.3-82.2	3	11.4-16.0	2.8-4.4
82.2-300	4	16.0-20.7	3.0-4.2
300-1090	5	20.7-25.3	3.1-4.1
1090-3920	6	25.3-29.8	3.2-4.0

Example

- ▶ String of inverters driving an off-chip load
 - ▶ Pad cap and load = 40pf
 - ▶ Equivalent to 20,000 microns of gate cap
 - ▶ Assume first inverter in chain has 7.2u of input cap
 - ▶ How many stages in inv chain?
- ▶ $H = 20,000/7.2 = 2777$
- ▶ From the table, 6 stages is best
- ▶ Stage effort = $f = (2777)^{1/6} = 3.75$
- ▶ Path delay $D = 6*3.75 + 6*P_{inv} = 28.5$
 - ▶ $D = 1.14\text{ns}$ if $\tau = 40\text{ps}$

Summary

- ▶ Compute path effort $F = GBH$
- ▶ Use table, or estimate $N = \log_4 F$ to decide on number of stages
- ▶ Estimate minimum possible delay
$$D = NF^{1/N} + \sum p_i$$
- ▶ Add or remove stages in your logic to get close to N
- ▶ Compute effort at each stage $f = F^{1/N}$
- ▶ Starting at output, work backwards to compute transistor sizes $C_{in} = (g_i/f)C_{out}$

Limits of Logical Effort

- ▶ Chicken and egg problem
 - ▶ Need path to compute G
 - ▶ But don't know number of stages without G
- ▶ Simplistic delay model
 - ▶ Neglects input rise time effects
- ▶ Interconnect
 - ▶ Iteration required in designs with wire
- ▶ Maximum speed only
 - ▶ Not minimum area/power for constrained delay

Summary

- ▶ Logical effort is useful for thinking of delay in circuits
 - ▶ Numeric logical effort characterizes gates
 - ▶ NANDs are faster than NORs in CMOS
 - ▶ Paths are fastest when effort delays are ~ 4
 - ▶ Path delay is weakly sensitive to stages, sizes
 - ▶ But using fewer stages doesn't mean faster paths
 - ▶ Delay of path is about $\log_4 F$ FO4 inverter delays
 - ▶ Inverters and NAND2 best for driving large caps
- ▶ Provides language for discussing fast circuits
 - ▶ But requires practice to master