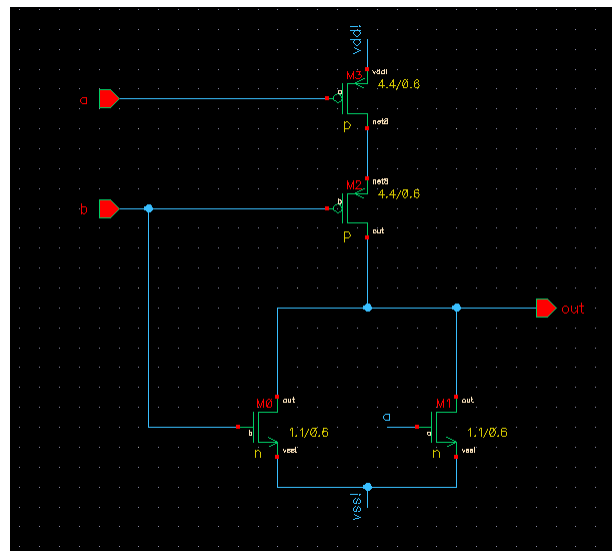


CS/EE 5710/6710

Layout
Basic Transistor Sizing
Intro to Verilog


An Example: NOR



► NOR schematic in Composer


First Layout: Follow Schematic



- ▶ Note that layout of transistors follows the schematic
 - ▶ Two P-types in series pulling up
 - ▶ Two N-types in parallel pulling down

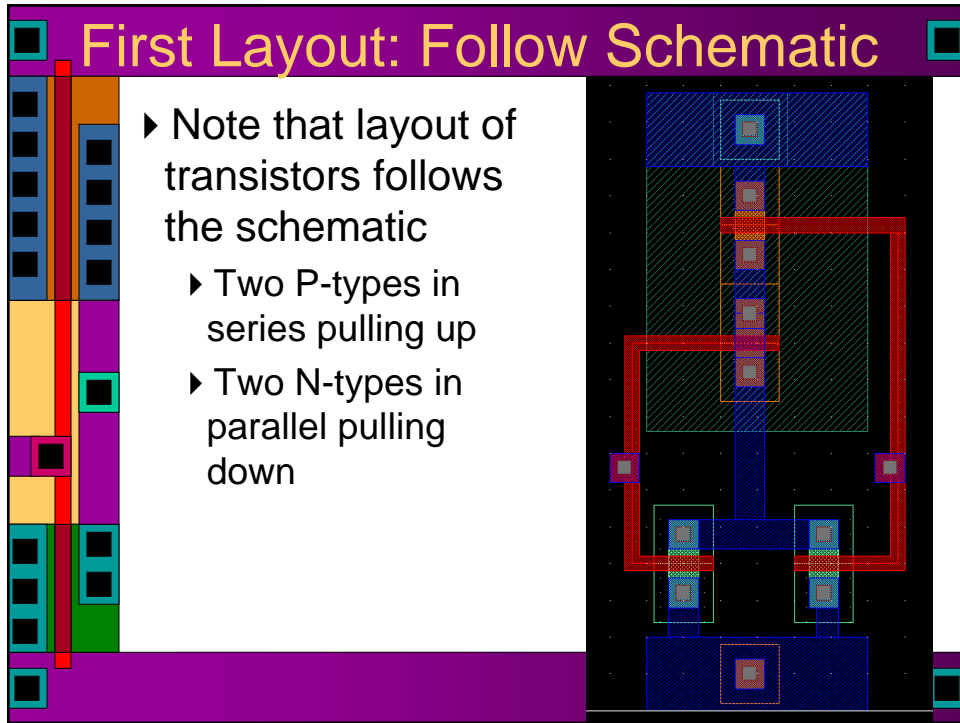
The image shows a circuit schematic on the left and its corresponding layout on the right. The schematic consists of a vertical stack of four transistors: two PMOS transistors in series at the top, and two NMOS transistors in parallel at the bottom. The layout on the right shows these transistors arranged in a similar vertical stack, with red lines representing the pull-up network and blue lines representing the pull-down network.

Another Layout: Better?

- ▶ Same four transistors
 - ▶ But, organized a little differently
 - ▶ And sized a little differently

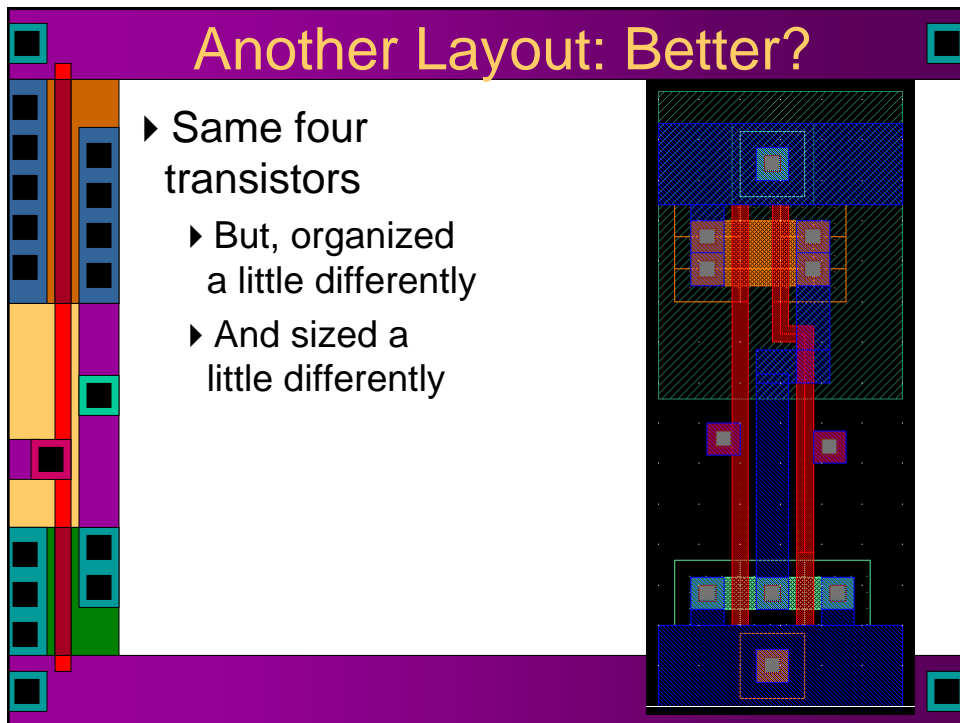The image shows a circuit schematic on the left and its corresponding layout on the right. The schematic is identical to the first layout, showing two PMOS transistors in series and two NMOS transistors in parallel. However, the layout on the right shows a different arrangement of the transistors, with the PMOS transistors placed side-by-side and the NMOS transistors also placed side-by-side, connected by a central vertical line. This layout is more compact and potentially more efficient than the first layout.

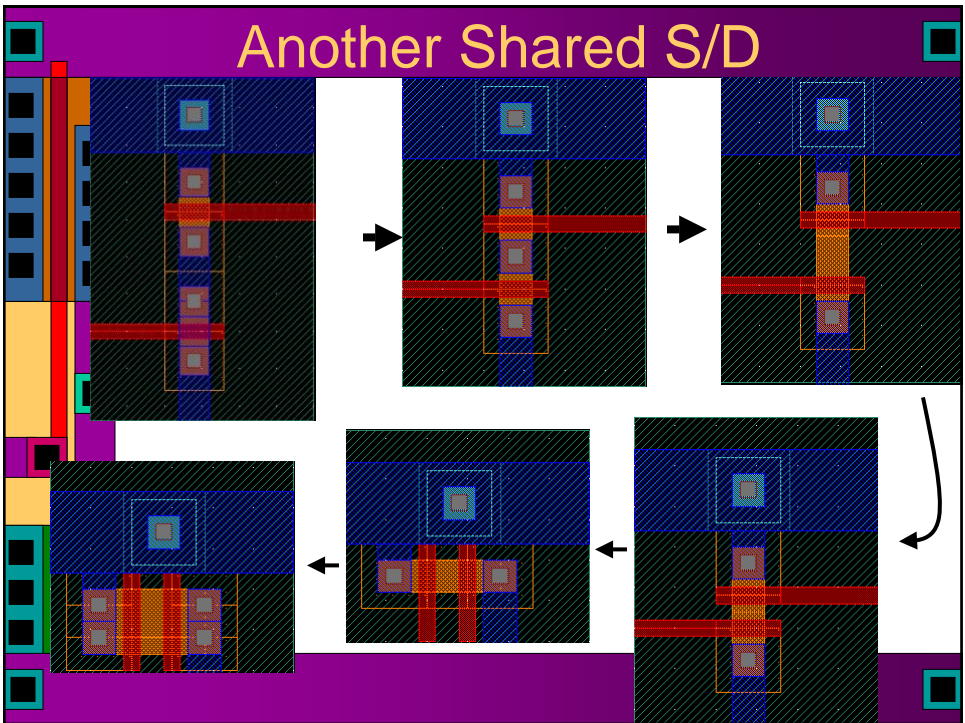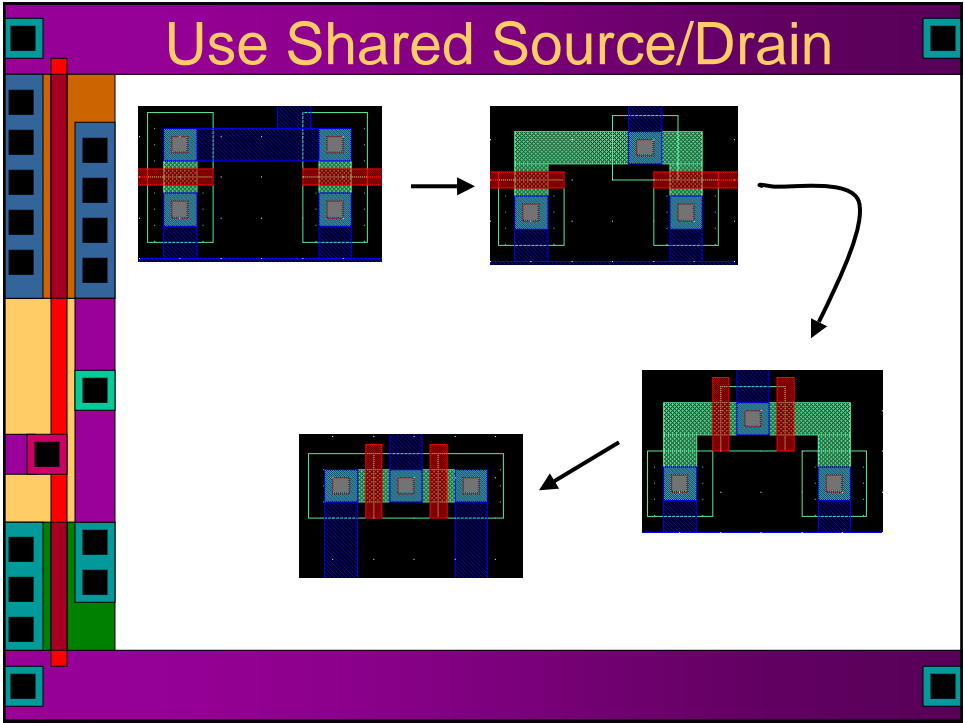


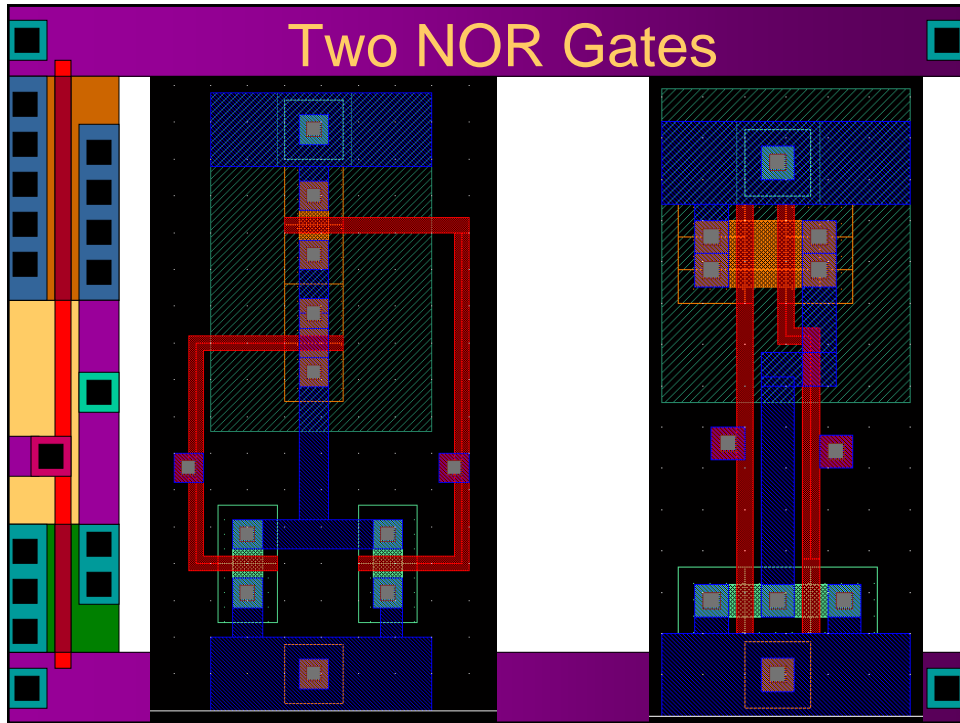


Transistor Sizing

- ▶ We'll get into the details later...
- ▶ Consider a transistor's Width and Length
 - ▶ Current capability is proportional to W/L
 - ▶ Length is almost always minimum allowed
 - ▶ Change width to change current capability



Sizing Rule of Thumb

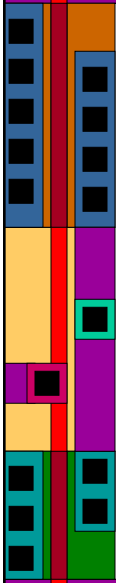- 
- ▶ Also, P-type is about twice as bad as N-type
 - ▶ Has to do with hole mobility vs. electron mobility
 - ▶ So, make P-types twice as wide as N-types to start with
 - ▶ Unit size for transistors this semester
 - ▶ N-type 1.2u (contact pitch)
 - ▶ P-type 2.4u

Sizing Rule of Thumb

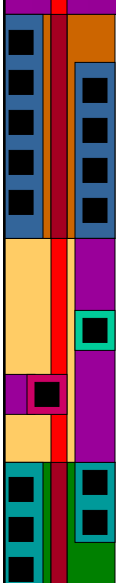
- 
- ▶ Now multiply each width by n for a series stack of n transistors.
 - ▶ Stack of 2, each transistor should be 2x unit size
 - ▶ Stack of 3, each transistor should be 3x unit size
 - ▶ This is because series connections are like increasing the L of the device...
 - ▶ Current is proportional to W/L

For example:

  

- ▶ Notice the difference in width...
- ▶ This roughly equalizes the current sourcing capability of pull-up and pull-down stacks in this gate

 And now for something completely different...



- ▶ A little Verilog...
- ▶ Big picture: Two main Hardware Description Languages (HDL) out there
 - ▶ VHDL
 - ▶ Designed by committee on request of the Department of Defense
 - ▶ Based on Ada
 - ▶ Verilog
 - ▶ Designed by a company for their own use
 - ▶ Based on C
- ▶ Both now have IEEE standards
- ▶ Both are in wide use

Data Types

- ▶ Possible Values:
 - ▶ 0: logic 0, false
 - ▶ 1: logic 1, true
 - ▶ X: unknown logic value
 - ▶ Z: High impedance state
- ▶ Registers and Nets are the main data types
- ▶ Integer, time, and real are used in behavioral modeling, and in simulation

Registers

- ▶ Abstract model of a data storage element
- ▶ A reg holds its value from one assignment to the next
 - ▶ The value “sticks”
- ▶ Register type declarations
 - ▶ `reg a; // a scalar register`
 - ▶ `reg [3:0] b; // a 4-bit vector register`

Nets

- ▶ Nets (wires) model physical connections
- ▶ They don't hold their value
 - ▶ They must be driven by a "driver" (i.e. a gate output or a continuous assignment)
 - ▶ Their value is Z if not driven
- ▶ Wire declarations
 - ▶ `wire d;` \\ a scalar wire
 - ▶ `wire [3:0] e;` \\ a 4-bit vector wire
- ▶ There are lots of types of regs and wires, but these are the basics...

Memories

- ▶ Verilog memory models are arrays of regs
- ▶ Each element in the memory is addressed by a single array index
- ▶ Memory declarations:
 - ▶ `reg [7:0] imem[0:255];` \\ a 256 word 8-bit memory
 - ▶ `reg [31:0] dmem[0:1023];` \\ a 1k word memory with 32-bit words

Other types

- ▶ Integers:
 - ▶ integer `i, j`; \ declare two scalar ints
 - ▶ integer `k[7:0]`; \ an array of 8 ints
- ▶ `$time` - returns simulation time
 - ▶ Useful inside `$display` and `$monitor` commands...

Number Representations

- ▶ Constant numbers can be decimal, hex, octal, or binary
- ▶ Two forms are available:
 - ▶ Simple decimal numbers: 45, 123, 49039...
 - ▶ `<size>'<base><number>`
 - ▶ base is d, h, o, or b
 - ▶ `4'b1001` // a 4-bit binary number
 - ▶ `8'h2fe4` // an 8-bit hex number

Relational Operators

- ▶ $A < B$, $A > B$, $A \leq B$, $A \geq B$, $A == B$, $A != B$
 - ▶ The result is 0 if the relation is false, 1 if the relation is true, X if either of the operands has any X's in the number
- ▶ $A === B$, $A !== B$
 - ▶ These require an exact match of numbers, X's and Z's included
- ▶ $!$, $\&\&$, $||$
 - ▶ Logical not, and, or of expressions
- ▶ $\{a, b[3:0]\}$ - example of concatenation

Block Structures

- ▶ Two types:
 - ▶ **always** // repeats until simulation is done
begin
...
end
 - ▶ **initial** // executed once at beginning of sim
begin
...
end

Example

- ▶ Reg [1:0] a,b;
initial begin // only executed once
 a = 2'b01; // initialize a
 b = 2'b10; // initialize b
end
always begin // repeated until simulation done
 #50 a = ~a; // a inverts every 50 time units
end
always begin // repeated until simulation done
 #100 b = ~b; // b inverts every 100 time units
end
- ▶ Note timing control: #50 = delay for 50 time units

Conditional, For

- ▶ If (<expr>) <statement> else <statement>
 - ▶ else is optional and binds with closest previous if that lacks an else
 - ▶ if (index > 0)
 if (rega > regb)
 result = rega;
 else
 result = regb;
- ▶ For is like C
 - ▶ for (initial; condition; step)
 - ▶ for (k=0; k<10; k=k+1)
 statement;

Basic Testbench

```
initial
begin
  a[1:0] = 2'b00;
  b[1:0] = 2'b00;
  cin = 1'b0;
  $display("Starting...");
  #20
  $display("A = %b, B = %b, c = %b, Sum = %b, Cout = %b", a, b, cin, sum, cout);
  if (sum != 00) $display("ERROR: Sum should be 00, is %b", sum);
  if (cout != 0) $display("ERROR: cout should be 0, is %b", cout);
  a = 2'b01;
  #20
  $display("A = %b, B = %b, c = %b, Sum = %b, Cout = %b", a, b, cin, sum, cout);
  if (sum != 00) $display("ERROR: Sum should be 01, is %b", sum);
  if (cout != 0) $display("ERROR: cout should be 0, is %b", cout);
  b = 2'b01;
  #20
  $display("A = %b, B = %b, c = %b, Sum = %b, Cout = %b", a, b, cin, sum, cout);
  if (sum != 10) $display("ERROR: Sum should be 10, is %b", sum);
  if (cout != 0) $display("ERROR: cout should be 0, is %b", cout);
  $display("...Done");
  $finish;
end
```

Nifty Testbench

```
reg [1:0] ainarray [0:4]; // define memory arrays to hold input and result
reg [1:0] binarray [0:4];
reg [2:0] resultsarray [0:4];
integer i;
initial begin
  $readmemb("ain.txt", ainarray); // read values into arrays from files
  $readmemb("bin.txt", binarray);
  $readmemb("results.txt", resultsarray);
  a[1:0] = 2'b00; // initialize inputs
  b[1:0] = 2'b00;
  cin = 1'b0;
  $display("Starting...");
  #10 $display("A = %b, B = %b, c = %b, Sum = %b, Cout = %b", a, b, cin, sum, cout);
  for (i=0; i<=4; i=i+1) // loop through all values in the memories
  begin
    a = ainarray[i]; // set the inputs from the memory arrays
    b = binarray[i];
    #10 $display("A = %b, B = %b, c = %b, Sum = %b, Cout = %b", a, b, cin, sum, cout);
    if ((cout,sum) != resultsarray[i])
      $display("Error: Sum should be %b, is %b instead", resultsarray[i],sum); // check results array
  end
  $display("...Done");
  $finish;
end
```